

Øving 4

Vsevolod Karpov - (vsevolok)

①

$$\textcircled{a) a) \quad V_o = V_i - V_L \\ \Rightarrow V_o = V_i - \frac{1}{sC} I(s)$$

$$V_o = I(s) \cdot R \Rightarrow V_i = I(s) \left(R + \frac{1}{sC} \right)$$

$$\Rightarrow H(s) = \frac{V_o}{V_i} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{CR}}$$

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{CR}}$$

$$\textcircled{a) b) \quad V_o = V_i - V_R \\ V_o = V_i - I(s) \cdot R$$

$$V_o = \frac{1}{sC} I(s) \Rightarrow V_i = \left(\frac{1}{sC} + R \right) \cdot I(s)$$

$$\Rightarrow H(s) = \frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1/RC}{s + \frac{1}{RC}}$$

$$H(j\omega) = \frac{1/RC}{j\omega + 1/RC}$$

$$\textcircled{a) c) \quad V_o = V_i - V_L$$

$$V_o = V_i - L \cdot s \cdot I(s), \quad V_o = I(s) \cdot R$$

$$\Rightarrow V_i = I(s)(R + L \cdot s)$$

$$\Rightarrow H(s) = \frac{R}{R + L \cdot s} = \frac{R/L}{R/L + s}$$

$$H(j\omega) = \frac{R/L}{R/L + j\omega}$$

a) d) $V_o = V_i - V_R$
 $V_o = V_i - I(s) \cdot R$

$$V_o = L \cdot s \cdot I(s) \Rightarrow V_i = I(s) (R + Ls)$$

$$\Rightarrow H(s) = \frac{Ls}{R + Ls} = \frac{s}{s + R/L}$$

$$H(j\omega) = \frac{j\omega}{j\omega + R/L}$$

b) a) $|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$

$$\Rightarrow |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}} = \frac{\omega^2 + j \frac{\omega}{RC}}{\omega^2 + (\frac{1}{RC})^2}$$

$$|H(j\omega)| = \frac{\sqrt{\omega^4 + \frac{\omega^2}{(RC)^2}}}{\omega^2 + (\frac{1}{RC})^2} = \frac{\omega}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$

$$\Rightarrow \frac{1}{\sqrt{2}} = \frac{\omega_c}{\sqrt{\omega_c^2 + (\frac{1}{RC})^2}} \Rightarrow \omega_c^2 + (\frac{1}{RC})^2 = 2\omega_c^2$$

$$\Rightarrow \omega_c = \frac{1}{RC}$$

b) b) $H(j\omega) = \frac{1/RC}{j\omega + \frac{1}{RC}} = \frac{\frac{1}{(RC)^2} - j \frac{\omega}{RC}}{\omega^2 + (\frac{1}{RC})^2}$

$$\Rightarrow |H(j\omega)| = \frac{\sqrt{\frac{1}{(RC)^4} + \frac{\omega^2}{(RC)^2}}}{\omega^2 + (\frac{1}{RC})^2} = \frac{1/RC}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$

$$\Rightarrow \frac{1/RC}{\sqrt{\omega_c^2 + (\frac{1}{RC})^2}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{(RC)^2} = \omega_c^2 + (\frac{1}{RC})^2$$

$$\Rightarrow \omega_c = \frac{1}{RC}$$

3

$$\textcircled{b} c) H(j\omega) = \frac{R/L}{R/L + j\omega} = \frac{(\frac{R}{L})^2 - j\frac{\omega R}{L}}{(\frac{R}{L})^2 + \omega^2}$$

$$\Rightarrow |H(j\omega)| = \frac{\sqrt{(\frac{R}{L})^4 + (\frac{\omega R}{L})^2}}{(\frac{R}{L})^2 + \omega^2} = \frac{R/L}{\sqrt{(\frac{R}{L})^2 + \omega^2}}$$

$$\Rightarrow \frac{1}{\sqrt{2}} = \frac{R/L}{\sqrt{(\frac{R}{L})^2 + \omega_c^2}} \Rightarrow \omega_c = \underline{\underline{R/L}}$$

$\textcircled{b} d)$ Same calculation as previously yields $\omega_c = \underline{\underline{R/L}}$

$\textcircled{c} a)$ High pass

b) Low pass

c) Low pass

d) High pass

$\textcircled{2}$

a) $f_c = 500 \text{ Hz}$

$$\omega_c = 500 \cdot 2\pi = \underline{\underline{1000\pi}}$$

$$\omega_c = \frac{1}{RC}, \quad \cancel{V_o = V_c} \quad V_{o\max} = 10 \text{ V}$$

$$V_{\omega_c} = \frac{1}{\sqrt{2}} \cdot V_{o\max}$$

$$P = \frac{V^2}{R} \Rightarrow Z = \frac{V_{\omega_c}^2}{R} \Rightarrow Z = \frac{1}{2} \cdot \frac{100}{R} \Rightarrow \underline{\underline{R = 25 \Omega}}$$

$$\Rightarrow C = \frac{1}{\omega_c R} = \underline{\underline{12.73 \mu\text{F}}}$$

$$\tau = RC = \underline{\underline{0.32 \text{ ms}}}, \quad \text{Bandwidth} = \underline{\underline{[500 \text{ Hz}, \infty]}}$$

③ a) KCL: $\frac{V_o - V_n}{R_2} + i_L = 0$

Ideal op-Amp $\Rightarrow V_n - V_p = 0$, $V_p = 0 \Rightarrow V_n = 0$

$\Rightarrow \frac{V_o(s)}{R_2} + I(s) = 0$

$V_i - V_n = i \cdot R_1 + \frac{1}{C} \cdot \int_0^t i(\tau) d\tau$
 $\Rightarrow V_i = I(s) \left(R_1 + \frac{1}{sC} \right)$

$\Rightarrow \frac{V_o(s)}{R_2} + \frac{V_i(s)}{R_1 + \frac{1}{sC}} = 0$

$\Rightarrow \frac{V_o(s)}{V_i(s)} = -R_2 \cdot \frac{1}{R_1 + \frac{1}{sC}} = -R_2 \cdot \frac{s}{R_1(s + \frac{1}{CR_1})}$

$R_1 = R_2 = 10 \text{ k}\Omega$, $C = 100 \mu\text{F}$

$\Rightarrow \underline{\underline{H(s) = -\frac{s}{s+1}}}$

$H(j\omega) = -\frac{j\omega}{j\omega + 1}$ (This is a H.P. inverting filter)

Since $\frac{R_1}{R_2} = 1$, amplification factor = 1
 and we can treat it as a passive filter where $\frac{1}{RC} = 1 \Rightarrow$

$\omega_c = \frac{1}{RC} = 1 \Rightarrow f_c = \frac{1}{2\pi} \text{ Hz} = \underline{\underline{0.16 \text{ Hz}}}$

Bandwidth: $[0.16 \text{ Hz}, \infty)$

④ a) $V_p = 0 \Rightarrow V_n = 0$

5

$$\text{KCL: } \frac{V_i - V_n}{R_1} + i_L = 0$$

$$\Rightarrow \frac{V_i(s)}{R_1} + I_L(s) = 0$$

$$i_L = \frac{V_o - V_n}{R_2} + i_c = \frac{V_o}{R_2} + C \cdot V_c'(t)$$

Since R_2 and C are in parallel: $V_c = V_o$

$$\Rightarrow i_L = \frac{V_o}{R_2} + C \cdot V_o'(t)$$

$$\Rightarrow I_L(s) = \frac{V_o(s)}{R_2} + Cs \cdot V_o(s) = V_o(s) \left(\frac{1}{R_2} + Cs \right)$$

$$\Rightarrow \frac{V_i(s)}{R_1} + V_o(s) \left(\frac{1}{R_2} + Cs \right) = 0$$

$$\Rightarrow \frac{V_o}{V_i} = - \frac{1}{R_1} \cdot \frac{1}{\left(\frac{1}{R_2} + Cs \right)} = - \frac{R_2}{R_1} \cdot \frac{1}{1 + CsR_2}$$

$$b) H(s) = - \frac{R_2}{R_1} \cdot \frac{1}{1 + CsR_2} = - \frac{1}{R_1 \cdot C} \cdot \frac{1}{\frac{1}{R_2 C} + s}$$

$$\Rightarrow H(j\omega) = - \frac{1}{R_1 \cdot C} \cdot \frac{1}{\frac{1}{R_2 C} + j\omega} \quad (\text{Low pass})$$

$$\Rightarrow H_{\max} = \frac{R_2}{R_1} \quad (|H(j\omega_0)|, \omega_0 = 0)$$

$$\Rightarrow \frac{R_2}{R_1} \cdot \frac{1}{\sqrt{2}} = |H(j\omega_c)| = \frac{1}{\sqrt{\left(\frac{1}{R_2 C} \right)^2 + \omega_c^2}} \cdot \frac{1}{R_1 C}$$

$$\Rightarrow \omega_c = \frac{1}{R_2 C}$$

c) $C = 100 \mu F$, $R_2 = 10 k\Omega$, $R_1 = \{1, 10, 100\} k\Omega$ 6

The corners are all at $\omega = \frac{1}{R_2 C}$, which is consistent with result from b).

(5)

a) $H_{hp}(s)$ is identical ~~with~~ to that found in 3a)

$$\Rightarrow H_{hp}(s) = -\frac{R_1}{R_1} \cdot \frac{s}{s + \frac{1}{C R_1}} = -\frac{s}{s + \omega_{hp}}$$

where $\omega_{hp} = \frac{1}{C R_1}$

b) $H_{lp}(s)$ is identical to that found in 4a)

$$\Rightarrow H_{lp}(s) = -\frac{R_2}{R_2} \cdot \frac{1}{1 + s \cdot R_2 C_2} = \frac{1/R_2 C_2}{1/R_2 C_2 + s}$$

$$= -\frac{\omega_{lp}}{\omega_{lp} + s}, \text{ where } \omega_{lp} = \frac{1}{R_2 C_2}$$

c) $H_{bp}(s) = H_{hp}(s) \cdot H_{lp}(s) = \frac{V_m}{V_i} \cdot \frac{V_o}{V_m} = \frac{V_o}{V_i}$

$$= -\frac{\omega_{lp}}{\omega_{lp} + s} \cdot -\frac{s}{s + \omega_{hp}} = \frac{\omega_{lp} \cdot s}{(\omega_{lp} + s)(\omega_{hp} + s)}$$

d) $R_1 = R_2 = 1000 \Omega$

7

$\omega_{hp} = 500 \text{ rad/s}$, $\omega_{lp} = 1000 \text{ rad/s}$


~~$H_{hp \text{ max}} = 1$~~
 ~~$\Rightarrow \frac{1}{2} =$~~

$\omega_{hp} = \frac{1}{C_1 R_1}$

$\Rightarrow C_1 = \frac{1}{\omega_{hp} \cdot R_1} = \underline{\underline{2 \mu F}}$

$C_2 = \frac{1}{\omega_{lp} \cdot R_2} = \underline{\underline{1 \mu F}}$

e)

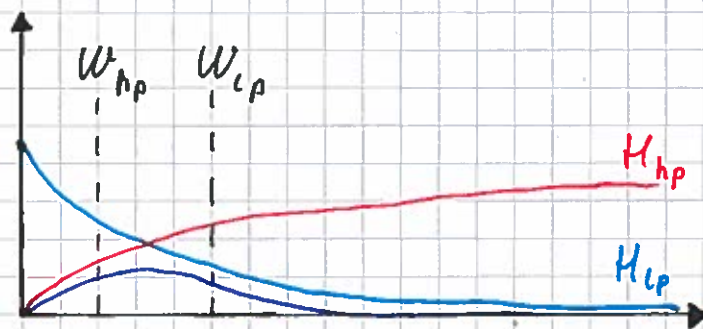

High pass passes frequencies higher than ω_{hp} , low pass passes frequencies lower than ω_{lp} . Combined, only frequencies with between ω_{hp} & ω_{lp} are passed. So, outside the $[\omega_{hp}, \omega_{lp}]$ band, the power transfer to the output is reduced by more than 50%.

Ergo: a band pass filter.